

# PROJECT

**CS/ECE/EEE/INSTR F241**

Microprocessor Programming & Interfacing

Batch No. 29

Question no. 22

## SPIRIT LEVEL REACTION TIME TESTER

### SUBMITTED BY

Adwait Bauskar	2014B4A7595G
Bharat Arora	2014B3A7629G
Abhiraj Saxena	2014B4A7680G
Shardul Walwadkar	2014B3A8798G
Shubham Agarwal	2014B4A7516G
Aaditya Vikas Vaze	2014B4A7603G



**BITS PILANI**  
**KK BIRLA GOA CAMPUS**

## Description

It is a Spirit Level Reaction Time Tester which is used for testing sobriety of a person. When the 'start' button is pressed, a random delay of time interval(4 – 8 seconds) is generated after which the first LED of the LED bar graph ( consisting of 9 LEDs) is lit after which the LEDs on the bar graph begin incrementing on a bar graph display so that they appear to 'rise' upwards. The user has to press the 'Stop' button as soon as she sees the LED bar rising.

The earlier the button pressed, fewer the LEDs lit and hence higher the sobriety. The entire bar graph of 9 LEDs will sweep to the top in 0.4 seconds (50ms delay between lighting of each LED) . The sobriety of a person on a scale of 1- 5 (1 – maximum intoxication) is displayed on a seven segment display according to the number of LEDs lit before the user has pressed the stop button.

## **Assumptions**

1. The person who is getting tested does not know the time when the spirit level tester is powered on.
2. Pressing of start button will be ignored until one test finishes completely.
3. Intoxication level is assumed to be linearly dependent on led lit before stop button.
4. Assuming debounce time is very less compared to one test time. hence no need to take debounce into consideration because start debounce happens in between the game(which will be ignored) and stop debounce will happen after the game (which also will be ignored).


## Components


COMPONENT	QTY
8086 Microprocessor	1
8255 Programmable Peripheral Interface	1
8253 Programmable Interval Timer	1
8284 Clock Generator	1
7 Segment Display	1
9 LED Bar Graph ( 9 LEDs)	1
74LS47 BCD to 7-Segment Decoder	1
74LS373 Octal transparent latch with 3 state outputs(8 bit buffers)	3
74LS245 Octal bus trans-receiver (2-way 8 bit buffers )	2
6116 RAM chip	2
2732 ROM chip	4
74LS00 AND gates	4
74LS02 OR gates	1
74LS32 NOT gates	1
74LS138 3:8 Decoder	3
Buttons	2
Resistors	3
100nF Capacitors	2
15 MHz crystal	1

# Interfacing


## I/O Interfacing

Component	Address
8255	00h-06h
8253	08h-0Eh

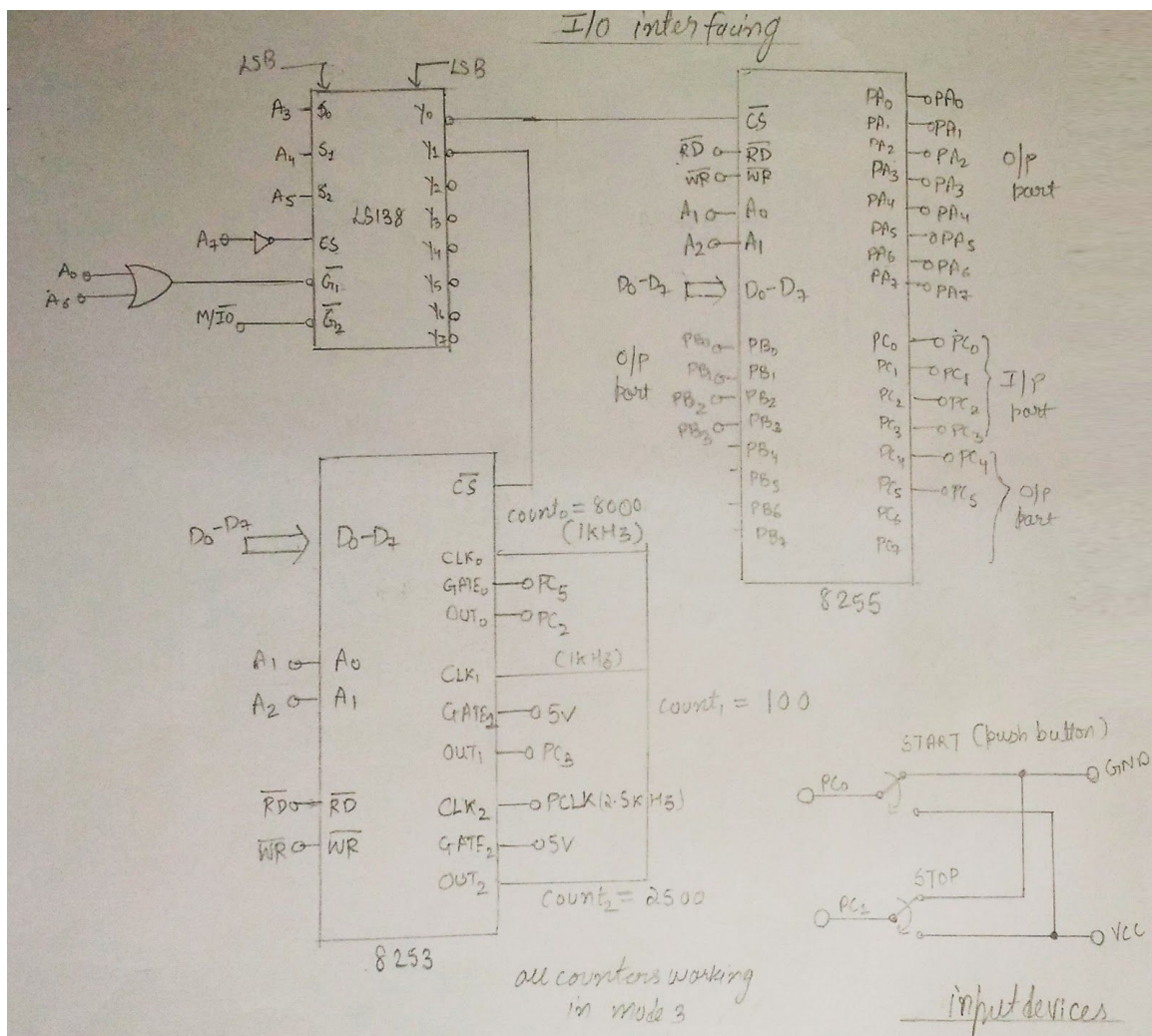

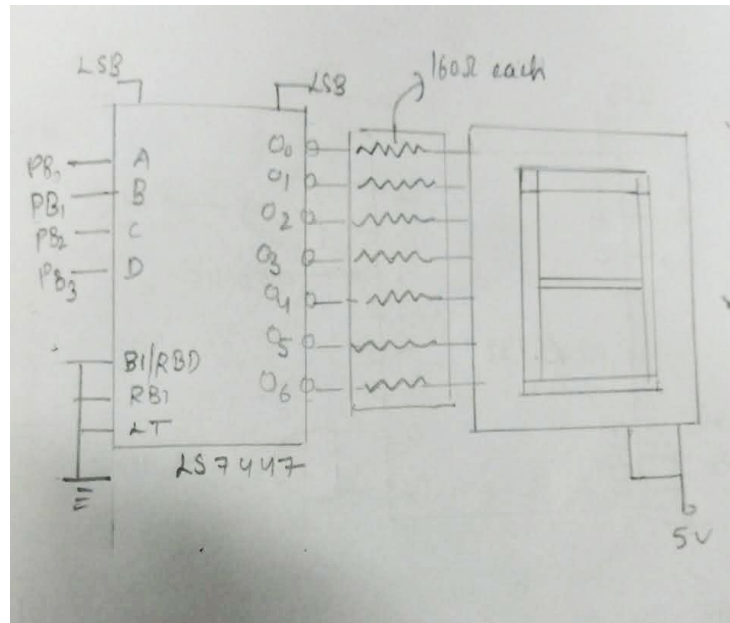


**7 Segment Display**

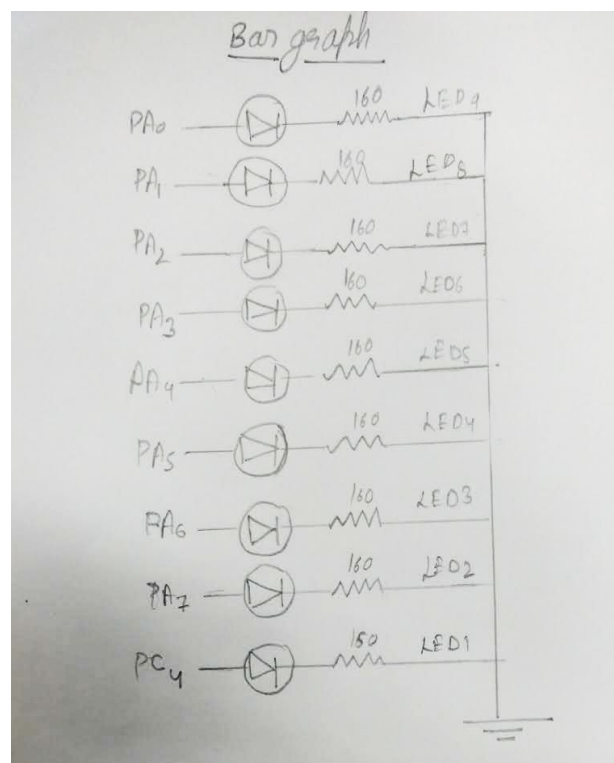

**LEDs**

## Data Interfacing

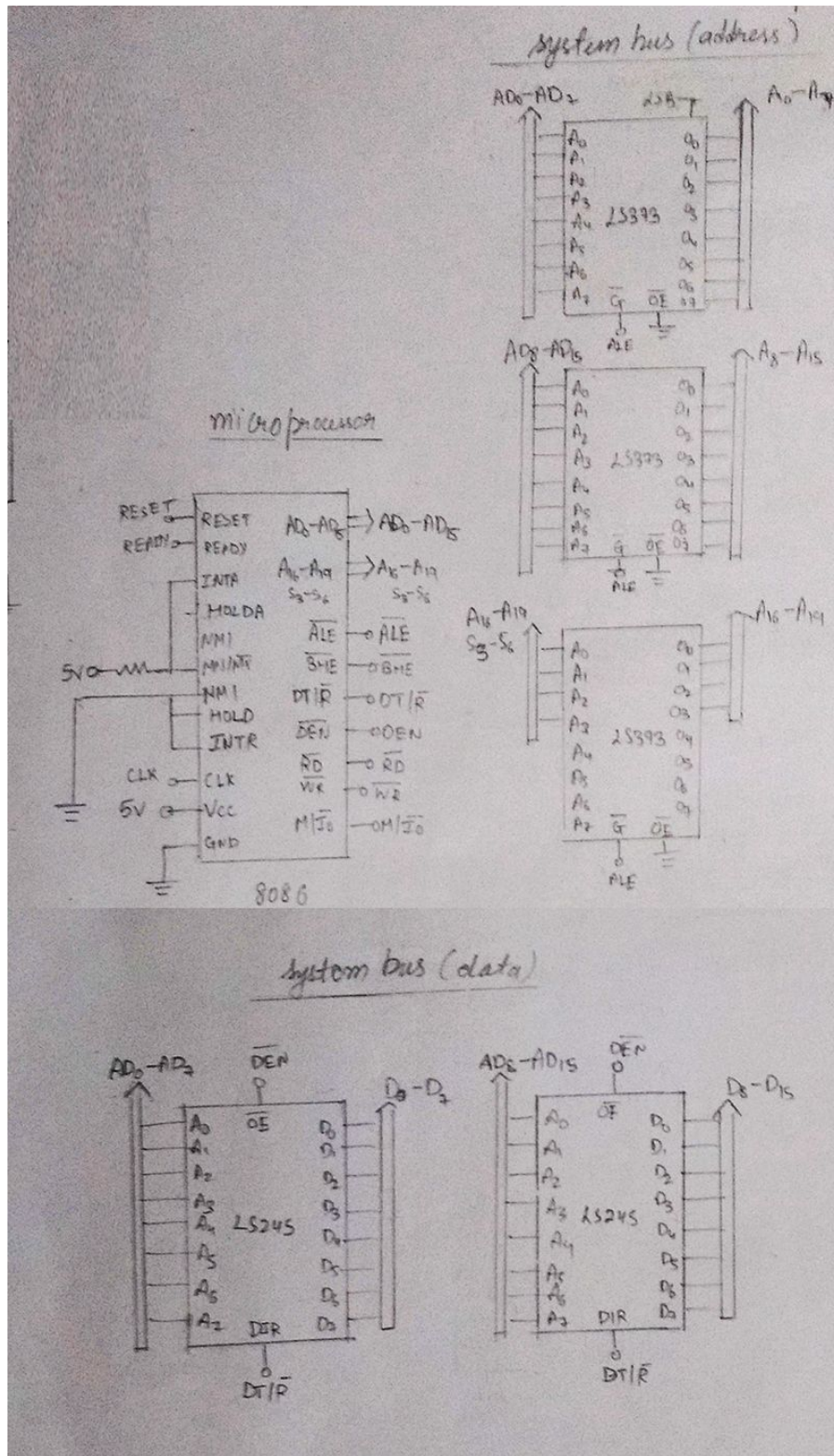




## Memory Interfacing

Component	Starting Address	Ending Address
ROM1	00000h	01FFFh
ROM2	FE000h	FFFFFh
RAM1	02000h	02FFFh

### Decoding Circuit

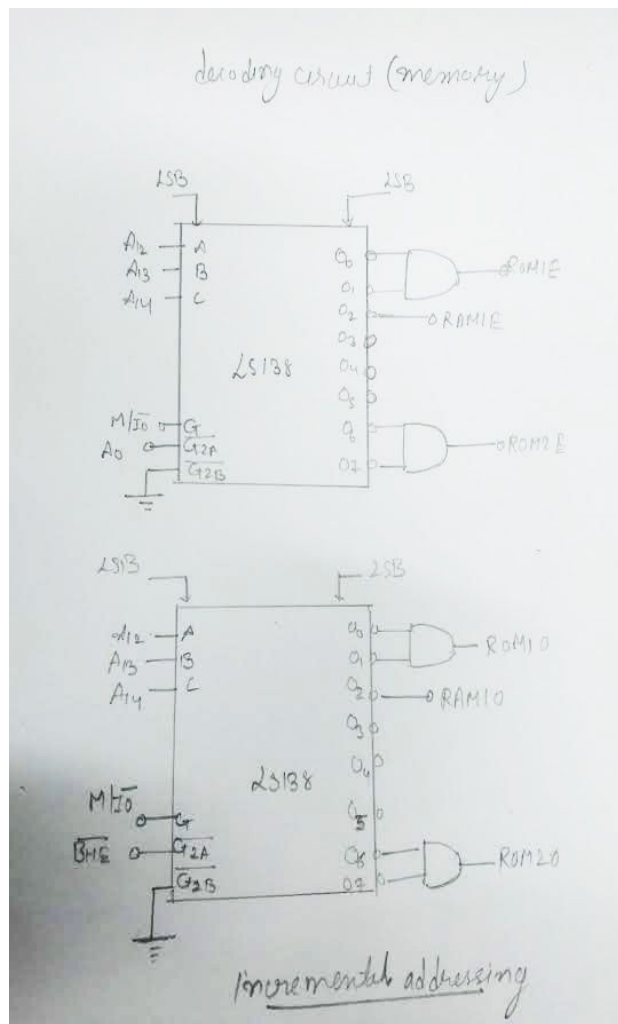



## Memory Mapping

